

Keywords: Tracking Power Supply Has Dual Outputs

## APPLICATION NOTE 1213

# Tracking Power Supply Has Dual Outputs

Sep 10, 2002

Designing a stable bipolar supply for powering op-amps, multiplexers, switches, etc. can be difficult, especially if the two voltages must track each other with respect to a non-zero or adjustable reference level. Such a regulated supply for low-power applications (**Figure 1**) produces a main-controller output voltage ( $V_{MAIN}$ ) and two tracking voltages symmetric about an adjustable reference voltage ( $V_{REF}$ ). You create the circuit by adding four Schottky diodes (D2–D5) and two flying capacitors (C2–C3) to the basic boost-converter circuit for U1.

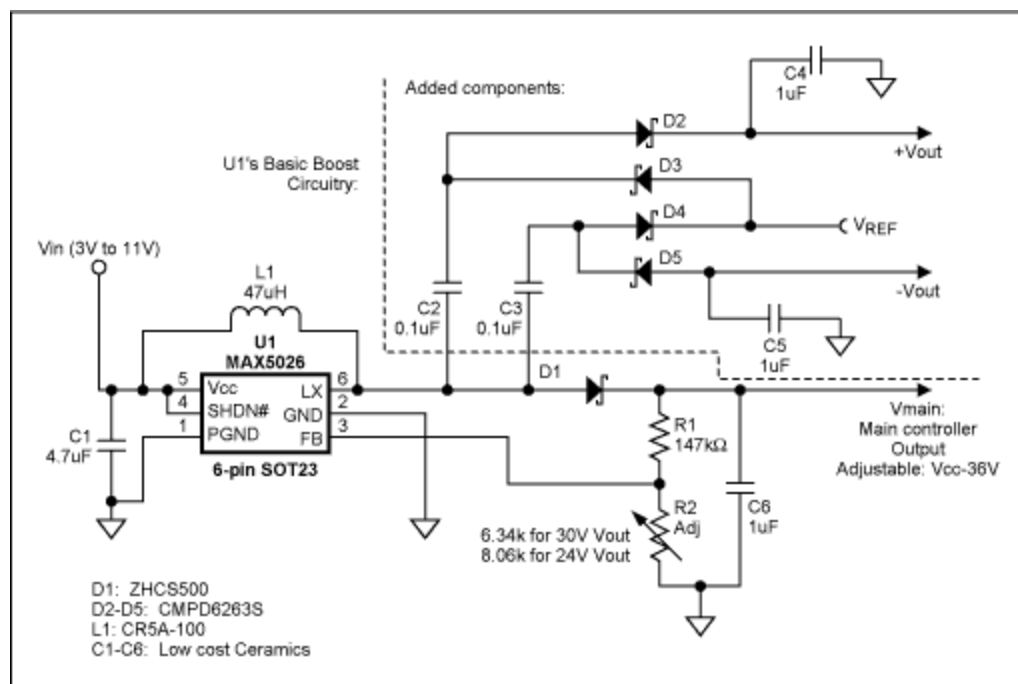


Figure 1. This single-IC circuit generates the bipolar voltages required in many industrial analog applications, as well as contrast-control voltages for an STN LCD.

U1 is an efficient, single-output boost converter for applications requiring outputs up to 36V and a wide input-voltage range (3V to 11V). U1 requires no external switching devices and draws a typical supply current of only 350 $\mu$ A, making it ideal for handheld and point-load applications. It is characterized for loads up to 120mW.

The  $\pm 30$ V outputs are centered about a reference level of  $V_{REF} = 0$ V (**Figure 2**). For balanced loads of

0.5mA to 2mA, tracking is excellent over a wide input range. **Figure 3** shows how  $+V_{OUT}$  and  $-V_{OUT}$  track each other as  $V_{REF}$  is moved away from 0V. One example of the need for a non-zero  $V_{REF}$  is indicated in **Figure 4**, in which the LCD-contrast voltages must be symmetric about  $V_{REF}$  to avoid a DC component across the liquid crystal, which in turn can damage the LCD or shorten its life.

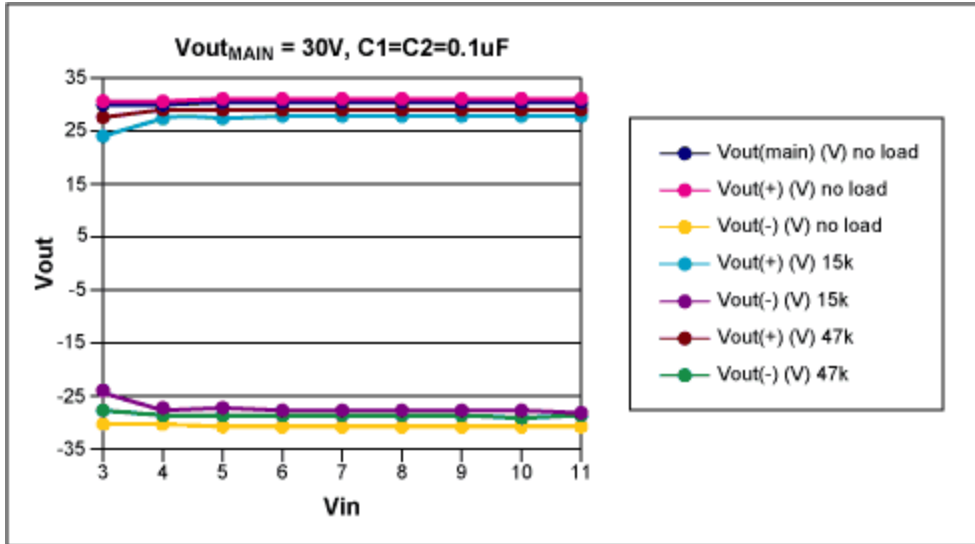


Figure 2. This graph shows the Figure 2 outputs of  $\pm V_{OUT}$  and  $V_{MAIN}$  across the full 3V–11V input voltage range, under varying load conditions.

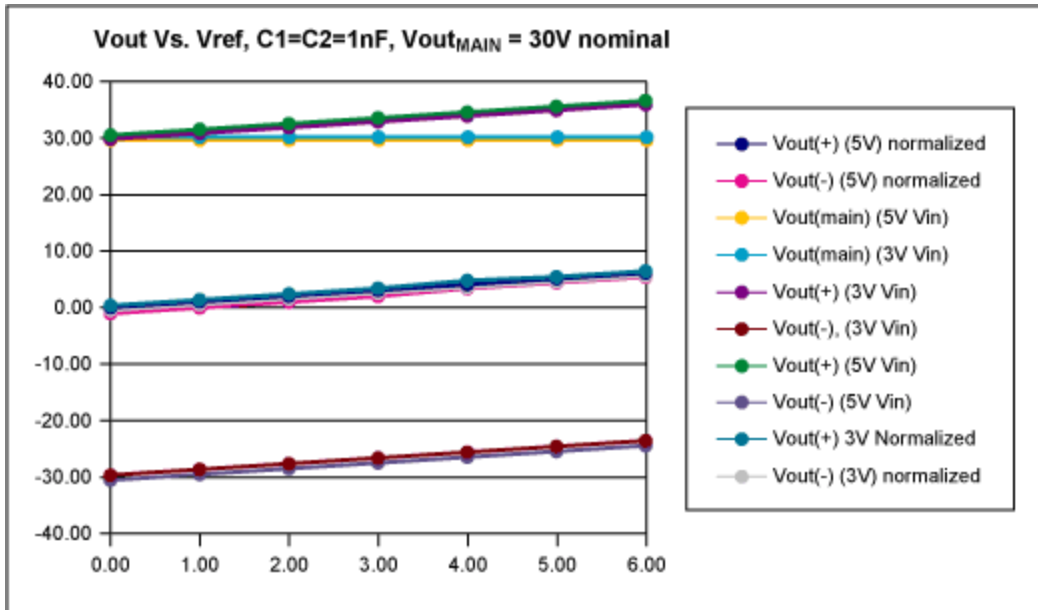


Figure 3. This graph shows that the  $\pm V_{OUT}$  outputs in Figure 1 track each other with respect to changes in the reference voltage:  $\pm V_{OUT} = V_{REF} \pm V_{MAIN}$ .

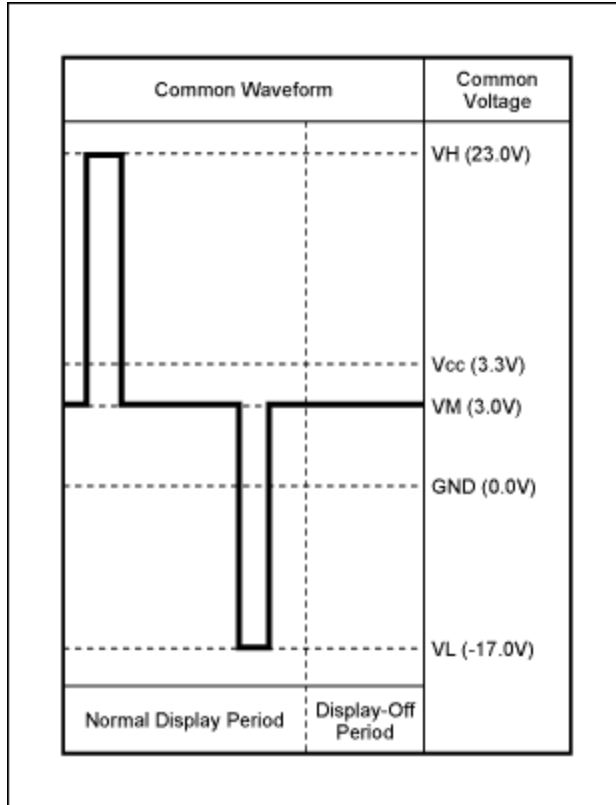


Figure 4. To avoid a damaging DC component across the LCD, these contrast waveforms are symmetrical about the reference level  $V_{REF}$ .

A FET internal to U1 repeatedly connects LX (pin 6) to ground and then releases it, causing the LX voltage to toggle between ground and  $V_{MAIN}$  plus one diode drop (D1). That action generates the  $\pm V_{OUT}$  voltages as follows:

**- $V_{OUT}$  output, phase 1:** The rise of LX voltage to  $V_{OUT} + V_{DIODE}$  forces voltage on the other side of C3 to  $V_{REF} + V_{DIODE}$ , creating a differential of  $V_{MAIN} - V_{REF}$  across C3. The LX node is our reference point. Phase 2: As LX is switched to ground, the load side ( $-V_{OUT}$ ) sees  $-V_{MAIN} + V_{REF}$ , forcing current from the  $-V_{OUT}$  load through D5, and the cycle repeats itself. Note that  $+V_{OUT}$  and  $-V_{OUT}$  develop on alternate phases. The resulting  $-V_{OUT}$  voltage is

$$-V_{OUT} = -V_{MAIN} + V_{REF} + V_{DIODE}.$$

**+ $V_{OUT}$  output, phase 2:** When LX is switched to ground, the load side of C2 sees  $V_{REF} - V_{DIODE}$ . Then, (phase 1) the rise of LX to  $V_{MAIN} + V_{DIODE}$  forces a voltage of  $V_{MAIN} + V_{REF}$  on the other side of C2. The resulting  $+V_{OUT}$  voltage is:

$$+V_{OUT} = V_{MAIN} + V_{REF} - V_{DIODE}.$$

These load equations suggest, and Figures 2 and 3 illustrate, that  $-V_{OUT}$  and  $+V_{OUT}$  track each other with respect to  $V_{MAIN}$ , and are offset by one diode drop from  $V_{REF}$ . D1–D5 are low-current Schottky diodes. C2 and C3 can be ceramic capacitors in the range 1nF to 100nF, preferably with voltage ratings of approximately  $2 \times |V_{OUT}|$ . Larger values of C2 and C3 provide more stable outputs under a wide range of load currents. L1 is typically 47 $\mu$ H, and the output capacitors C4–C6 (shown with 1 $\mu$ F values)

may be sized according to the allowable output ripple.

A similar version of this article appeared in the July 15, 2002 issue of *Planet Analog* magazine.

#### Related Parts

<a href="#">MAX5026</a>	500kHz, 36V Output, SOT23, PWM Step-Up DC-DC Converters	<a href="#">Free Samples</a>
-------------------------	---	------------------------------

---

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 1213: <http://www.maximintegrated.com/an1213>

APPLICATION NOTE 1213, AN1213, AN 1213, APP1213, Appnote1213, Appnote 1213

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>